

Digital and Comp Org: Another Perspective

By. Poksin Wanchawee

CPE Student, KU

October 3, 2019

About me

Poksin Wanchawee

- Taeyeon CPE31 , Hwang Jisung
- Computer Engineer Student, Kasetsart University
- Interesting in computer system and computer architecture
- Love K-pop [Wanna One / NU'EST / X1 's fanboy]

How do computers really work??

- A question in my mind ...
- That's why i wanted to learn in computer major... so, I study here
- computer architecture answers me 70% of what i'm curious



Outline

- Basic Digital Design
 - Combinational logic circuit / Sequential logic circuit
 - ALU / Memory (RAM,ROM,Register)
 - Logism
- Processor design and simulation
 - ISA (Instruction Set Architect) : Minimal MIPS
 - Minimal MIPS Datapath
 - Real Word Architect : MIPS x86

Basic Digital Design

Combinational Logic Circuit

  - A circuit is a network that processes discrete-valued variables, can be viewed as a black block.
- Combinational circuit's output depends only on the current value.
- Boolean equations are perfect for describing digital logic.
 - Sum-of-Product
 - Product-of-Sum
- Boolean algebra are used to simplify boolean expression
 - Axioms table
 - K-map



Typical
Truth Table

C	B	A	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Figure from https://www.electronics-tutorials.ws/combination/comb_1.html

Classification of Combinational Logic Circuit





- Arithmetic & Logical Function
 - ALU in processor
- Data Transmission
 - MUX / DEMUX
 - Encoder / Decoder
- Code Converter
 - 7-segment
- Any Function
 - $F(\text{Input}) = \text{Output}$

Arithmetic & Logic Function

- Adder
 - Half / Full / Carry Propagate / Ripple-carry / Carry-Lookahead
- Subtractor
- Comparator

Data Transmission & Code Convertor

    - MUX/DEMUX
 - MUX 2 power n inputs, 1 output : Shannon's equation
 - DEMUX 1 input, 2 power n outputs
- Decoder/Encoder
- 7 segment



Inputs				Outputs	
D ₃	D ₂	D ₁	D ₀	Q ₁	Q ₀
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1
0	0	0	0	x	x

Figure from https://www.electronics-tutorials.ws/sequential/seq_1.html
<https://www.geeksforgeeks.org/digital-electronics-bcd-7-segment-decoder/>

Hardware Description Language


- The language to describe hardware in Module
- HDL is a specialized computer language used to describe the structure and behavior of electronic circuits, and most commonly, digital logic circuits.
[Wikipedia]
- VHDL and System Verilog

Try to play : 4-bits Simple ALU

- Combining arithmetic & logic function, data transmission and code converter to simple ALU circuit
- ALU = Arithmetic & Logic Unit : essential to use for executing in processor

Sequential Logic Circuit

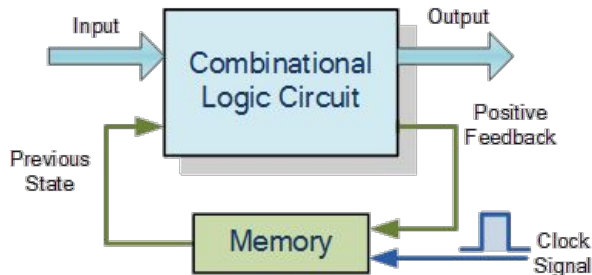- Unlike Combinational Logic circuits that change state depending upon the actual signals being applied to their inputs at that time, Sequential Logic circuits have some form of inherent “Memory” built in.
- Synchronous Sequential Logic Circuit deals with Clock signal
- Latch and Flip-Flop are basic “Memory” element.
 - Keep the state
- Synchronus Design Method : FSM (Mearly/Moore)



Latch/Flip-Flop and Register

- bistable element, an element with two stable states
- Flip-Flop [D Flip-Flop, T Flip-Flop, JK Flip-Flop]
- D Flip-Flop can be built from two back-to-back D latches controlled by complementary clock
 - In this slide, I will mention a detail only D flip/flop
- Register is a bank of D Flip-Flop share a common CLK
 - so that all bits are updated on the same time

 


Figure 3.7 D latch: (a) schematic, (b) truth table, (c) symbol

Figure from David Money H. & Sarah L.H. ,Digital Design and Computer Architecture (2nd Edition)


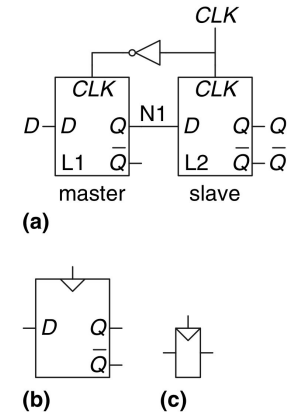


Figure 3.8 D flip-flop:
(a) schematic, (b) symbol,
(c) condensed symbol

Counter / Shifter

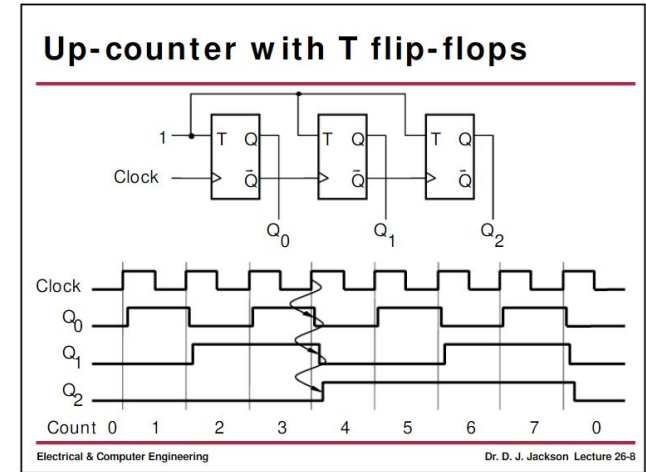- Use flip-flop (and also clock signal) to implement
- Counter
 - To increment or decrement by 1
 - Often use T flip-flop because a toggle feature
- Shifter



Memory

- Register : a bank of D Flip-Flop share a common CLK
- ROM : Read-Only Memory
 - Control Unit of processor
- RAM : Random Access Memory
 - Memory unit in processor

n bit Register file

- a set of n registers size 32 bits
- MIPS first hierarchy memory
 - close to processor the most

FIGURE C.8.7 A register file with two read ports and one write port has five inputs and two outputs. The control input Write is shown in color.

 


FIGURE C.8.8 The implementation of two read ports for a register file with n registers can be done with a pair of n -to-1 multiplexors, each 32 bits wide. The register read number signal is used as the multiplexor selector signal. Figure C.8.9 shows how the write port is implemented.

Try to play : 4-bits Simple ALU with Input Memory

- Combining arithmetic & logic function, data transmission and code converter to simple ALU circuit
- Including “Memory” keeping the input. Output changes every falling edge trigger

Processor design and simulation

Processor

- Essential computing components of computer
- Basically consists of ALU , Memory and Control Unit

 


Figure from <https://www.it4nextgen.com/what-is-a-cpu-central-processing-unit/>

Instruction Set Architecture

- If we have any processor (in form black box), how can you instruct it to do on your demand... what you would like instruct it... it's instruction ...
- An instruction set architecture (ISA) is an abstract model of a computer. It is also referred to as architecture or computer architecture.
- A realization of an ISA is called an implementation. (Wikipedia)

MIPS ISA

- 32-bit Instruction (32-bit 0f 01's)

R-type

op	rs	rt	rd	shamt	funct
----	----	----	----	-------	-------

 add \$1, \$2, \$3
Arithmetic instruction format

I-type

op	rs	rt	address/immediate
----	----	----	-------------------

 addi \$1, \$2, 0x10
Transfer, branch, immediate.


J-type

op	target address
----	----------------

 j 0x00000010
Jump instruction

Field size

6 bits	5bits	5bits	5bits	5bits	6 bits
--------	-------	-------	-------	-------	--------




More detail in
01204225 >>

Minimal MIPS Processor

- Minimal version of MIPS (define for this lecture only)
 - MIPS (Microprocessor without Interlocked Pipelined Stages) is a reduced instruction set computer (RISC) instruction set architecture (ISA)
 - detail more in 01204225
- consists of only 5 instructions
 - addu / addiu
 - beq
 - and / andi
- MIPS assembly
 - addu \$1, \$2, \$3 # \$1 = \$2 + \$3
 - addiu \$1, \$2, 0x10 # \$1 = \$2 + 0x10
 - beq \$1, \$2, 0xf8 # branch to PC = PC+4+0xf8 if \$1 == \$2
 - and \$1, \$2, \$3 # \$1 = \$2 && \$3 (bitwise)
 - andi \$1, \$2, 0x10 # \$1 = \$2 && 0x10 (bitwise)

Minimal MIPS single cycle datapath

- 1 instruction per 1 clock cycle

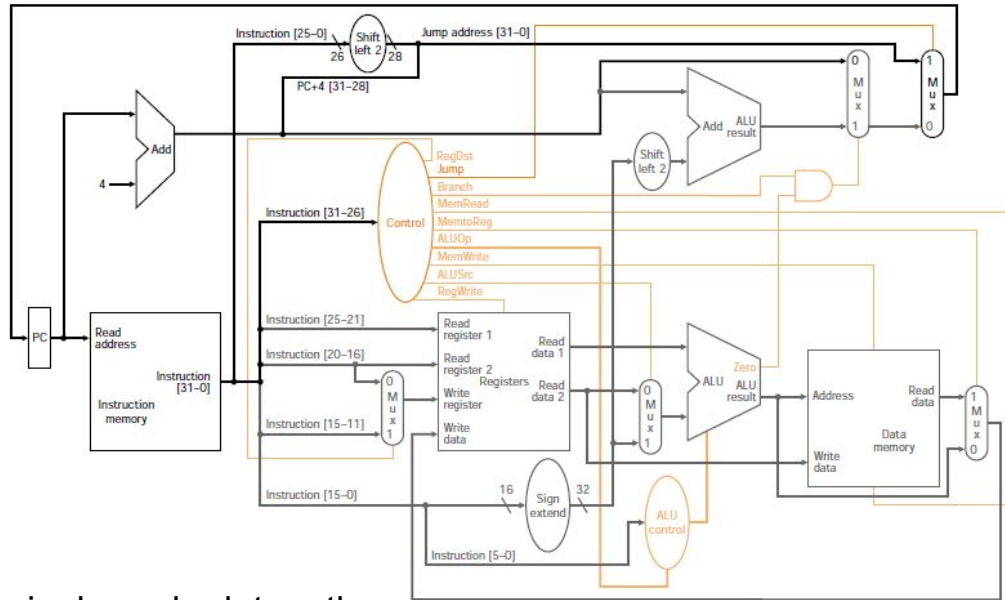

More detail in
01204225 >>

Design a single cycle datapath

https://cseweb.ucsd.edu/classes/su06/cse141/slides/s05-1cyc_data-1up.pdf

Try to implement : Processor implementation

Download mininal_MIPS_single_cycle on <http://bit.ly/2pvuG2E>

, then follow me to implement

Real Life Architecture

- MIPS
- ARM : Advance RISC Machine
 - Microprocessor and microcontroller
- X86 : Intel CPU More detail >> <https://cs.lmu.edu/~ray/notes/x86overview/>

ARM Instruction Set Format

2827				1615				87				0				Instruction type											
Cond	0	0	1	Opcode				S	Rn	Rd				Operand2				Data processing / PSR Transfer									
Cond	0	0	0	0	0	0	0	A	S	Rd	Rn	Rs	1	0	0	1	Rm	Multiply									
Cond	0	0	0	0	1	U	A	S	RdHi	RdLo	Rs	1	0	0	1	Rm	Long Multiply (v3M / v4 only)										
Cond	0	0	0	1	0	B	0	0	Rn	Rd	0	0	0	0	1	0	0	1	Rm	Swap							
Cond	0	1	1	F	U	B	W	L	Rn	Rd	Offset								Load/Store Byte/Word								
Cond	1	0	0	F	U	S	W	L	Rn	Register List										Load/Store Multiple							
Cond	0	0	0	F	U	l	W	L	Rn	Rd	Offset1	1	S	H	1	Offset2	Halfword transfer : Immediate offset (v4 only)										
Cond	0	0	0	F	U	0	W	L	Rn	Rd	0	0	0	0	1	S	H	1	Rm	Halfword transfer: Register offset (v4 only)							
Cond	1	0	1	Offset												Branch											
Cond	0	0	0	1	0	0	1	0	1	1	1	1	1	1	1	1	1	1	0	0	0	1	Rn	Branch Exchange (v4T only)			
Cond	1	1	0	F	U	N	W	L	Rn	CRd	CPNum	Offset										Coprocessor data transfer					
Cond	1	1	1	0	Op1				CRn	CRd	CPNum	Op2	0	CRm				Coprocessor data operation									
Cond	1	1	1	0	Op1				L	CRn	Rd	CPNum	Op2	1	CRm				Coprocessor register transfer								
Cond	1	1	1	1	SWI Number												Software interrupt										

Textbook I recommend

- David Money H. & Sarah L.H. ,Digital Design and Computer Architecture (2nd Edition)
- M. Morris M. & Michael D. C ,Digital Design With An Introduction to the Verilog HDL (5th Edition)
- David A. P. & John L. H. ,Compter Organization and Design (5th Edition)